

PROBLEM 13.1

Find the Thévenin voltage and resistance for the circuit shown.

