

# FIGURE 1.14.8 (a)

FIGURE 1.14.8 (a) shows the circuit diagram of a two-stage amplifier. The first stage is a common-emitter amplifier with a voltage divider bias network. The second stage is a common-emitter amplifier with a voltage divider bias network. The output of the second stage is connected to a load resistor.

