

# PROBLEM 1.3.1

Find the current  $i$  in the circuit shown.

