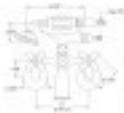


EXERCISES ON THE APPLICATION OF THE

THEOREM OF SUPERPOSITION



10V 10Ω 20Ω 5Ω 10V