

FIGURE 12-10

Illustration of a simple two-stage transistor amplifier.

