

## QUESTION 2 (5 Marks)

Consider the following circuit diagram.

