



The diagram illustrates a three-phase power system. It shows three vertical lines representing phases, labeled "Phase 1", "Phase 2", and "Phase 3" from left to right. Each phase line is connected to a corresponding busbar at the top. The busbars are connected to a central point, likely a transformer or generator. Below the busbars, there are three separate vertical lines, each connected to one of the busbars, representing the output or distribution lines for each phase.

QUESTION



The diagram illustrates a three-phase power system. It shows three vertical lines representing phases, labeled "Phase 1", "Phase 2", and "Phase 3" from left to right. Each phase line is connected to a corresponding busbar at the top. The busbars are connected to a central point, likely a transformer or generator. Below the busbars, there are three separate vertical lines, each connected to one of the busbars, representing the output or distribution lines for each phase.