

## PROBLEM 2.8

For the circuit shown, find the average power absorbed by the load.

