

PROBLEM 1

Consider the circuit shown below.



Find the current i in the circuit.

