

## QUESTION 1

Figure 1 shows the arrangement of the four arms of a Wheatstone bridge. The bridge is used to measure the resistance of a component,  $R_x$ .



Figure 1



Figure 2