

PROBLEM 2.3.10

Find the current i in the circuit.

