

# PROBLEM 11.10

Find the Thévenin voltage and Thévenin resistance for the circuit shown.

