

QUESTION 2 (10%)

Consider the circuit shown below. Assume that the diodes are ideal.

