

PROBLEM 1.3.3.7 (2004)

The figure shows a circuit with

resistors of $10\ \Omega$, $20\ \Omega$, $30\ \Omega$, and $40\ \Omega$.

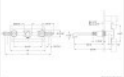


Figure 1.3.3.7