

# PROBLEM 1.7

Find the power in the 20- $\Omega$  resistor.

