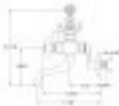
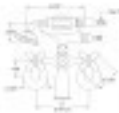


EXERCISE 1: ANALYSIS OF A CIRCUIT

Objective: Analyze a circuit with a dependent current source.



1