

PROBLEM 1

Consider the following circuit diagram:

