

PROBLEM 2 (100 pts)

Consider the circuit shown below.

Find the power dissipated in the 2 ohm resistor.

