

# EXERCISE 13.56 14

1. The circuit is shown in the figure below.

