

# QUESTION 13

Which of the following is a correct circuit diagram for a parallel circuit?

