



1. The circuit is complete when the switch is closed. The bulb will glow.

2. The circuit is incomplete when the switch is open. The bulb will not glow.

3. The circuit is complete when the switch is closed. The bulb will glow.

4. The circuit is incomplete when the switch is open. The bulb will not glow.

© 2010 Pearson Education, Inc. or its affiliate(s). All rights reserved.



© 2010 Pearson Education, Inc. or its affiliate(s). All rights reserved.