

QUESTION

10. The following circuit is a common-emitter amplifier. The input signal is $v_{in}(t) = 0.1 \cos(2000\pi t)$ V. The output signal is $v_{out}(t) = 10 \cos(2000\pi t + \phi)$ V. The phase shift ϕ is:

