

## QUESTION 1 (3.0/3.750)

For a circuit with  $R = 100 \Omega$

and  $V = 100 \text{ V}$ , find the power  $P$ .

