

# PROBLEM

1. A circuit is shown in the figure below. Find the current  $i$  through the  $2\ \Omega$  resistor.



1