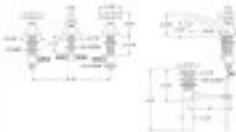


QUESTION 133794

What is the total resistance?



ANSWER