

FIGURE 1.14

Block diagram of a two-stage amplifier.

