



1. The circuit is complete when the switch is closed.

2. The bulb will glow when the switch is closed.

3. The bulb will not glow when the switch is open.

4. The bulb will glow when the switch is closed.

5. The bulb will not glow when the switch is open.

6. The bulb will glow when the switch is closed.



7. The bulb will glow when the switch is closed.