

QUESTION

1. The following circuit is a typical example of a **_____**.



ANSWER