

## PROBLEM 2.10 (continued)

For the circuit shown in Fig. 2.10, find  $i_1$ ,  $i_2$ , and  $i_3$ .

