

# PROB 1.2 (10%)

Using the circuit below, determine the power dissipated in the 100 Ω resistor.

