

# EXERCISES ON THE ANALYSIS OF CIRCUITS

1. Calculate the power dissipated in the circuit.

