

# PROBLEM 2.5.10

Find the current  $i$  in the circuit.

