

EXERCISE 1: ANALYSIS OF A CIRCUIT

Objective: Analyze the circuit and determine the power dissipated in the resistor.

