

EXERCISE 1.2.3 (7 min)

The circuit diagram of a power supply is shown in the figure.

