

## QUESTION 1

Figure 1 shows a circuit diagram of a transformer with a primary winding of 100 turns and a secondary winding of 200 turns. The primary winding is connected to an AC source of 230 V. The secondary winding is connected to a load resistor of 10  $\Omega$ . The transformer is ideal.

