

PROB 1.5Y1

Use the circuit diagram to answer the questions.



Figure 1