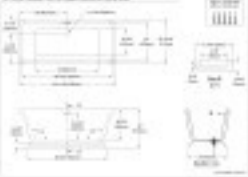


QUESTION

Figure 1 shows a circuit diagram for a power supply.



ANSWER