

# PROBLEM 1

Consider the following circuit diagram.

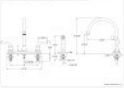


Figure 1