

QUESTION 26 (10)

Refer to the circuit below. The value of R_2 is _____ Ω .

