

PROBLEM 1.10

Find the current i in the circuit shown in Fig. 1.10.

