

WIRING FOR LAMP AND TUBE TESTS

Connect the circuit as shown in the diagram below.

