

PROBLEM 2 (10%)

Consider the following circuit diagram.

