

# PROBLEM 1.3 (40 points)

Consider the circuit shown below. The circuit is a bridge circuit with a central branch.

