

2012 AP Physics 2

1. A circuit is shown in the diagram below. The battery has an emf of \mathcal{E} and negligible internal resistance. The resistors have resistances R and $2R$. The capacitor has a capacitance of C . The switch is initially open. The circuit is then closed.

