

PROBLEM 1

For the circuit shown, determine the power dissipated in the 10 Ω resistor.

