

1. **Identify the components of the circuit.**
The circuit consists of a battery, a resistor, and a light bulb.



2. **Calculate the current flowing through the circuit.**

