

EXAMPLE 3.10

Find the Thévenin voltage and Thévenin resistance of the circuit in Fig. 3.10.

