

QUESTION 2 (10 Marks)

The following diagram shows a circuit used to determine the internal resistance of a cell.

