

EXERCISES ON THE ANALYSIS OF CIRCUITS

1. Calculate the power dissipated in the resistor in the circuit shown below.

