

# PROBLEM 2-4.67 (25)

Two identical 100-ohm resistors are connected in parallel.

